Analog Circuits

Assignment – II

(1) → Draw the circuit diagram of voltage series, voltage shunt, current series & current shunt feedback Amplifiers and calculate the input resistance ?

(2) → List out the various characteristics of Negative feedback Amplifiers and prove how the stability increases ?

(3) → Define oscillator and mention the conditions for oscillations ?

(4) → Draw the ckt diagram of Wein bridge oscillator and calculate its frequency of oscillations ?

(5) → Explain the operation of colpitts oscillator and derive the frequency of oscillations.

(6) → Explain the operation of LC tank ckt in oscillators and write the expression for frequency of oscillation of Hartly oscillators ?

Scanned with OKEN Scanner